

1. Design a double-stub impedance matching circuit for  $Z_L = (12.5 - 37.5j)\Omega$  in ADS. The stubs are open-circuited stubs and are spaced  $\lambda/8$  apart. The operation frequency is at 2.4 GHz. Plot the reflection coefficient spectrum from 1 to 5 GHz.
2. Plot the input impedance (magnitude and phase) spectrum and reflection coefficient spectrum from 1 GHz to 10 GHz for different parallel RLC circuits including (a)  $R = 50\Omega$ ,  $L = 0.25$  nH,  $C = 4$  pF, (b)  $R = 50\Omega$ ,  $L = 4$  nH,  $C = 0.25$  pF, (c)  $R = 200\Omega$ ,  $L = 1$  nH,  $C = 1$  pF. Discuss the quality factor, reflection coefficient, and phase changes near resonant frequency for these three cases.