
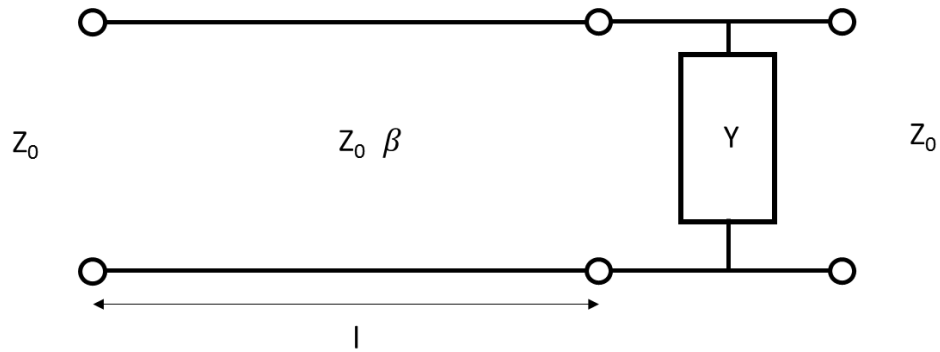


HW10 due to 12/14 (submit online at NTUCOOL before 9 am)

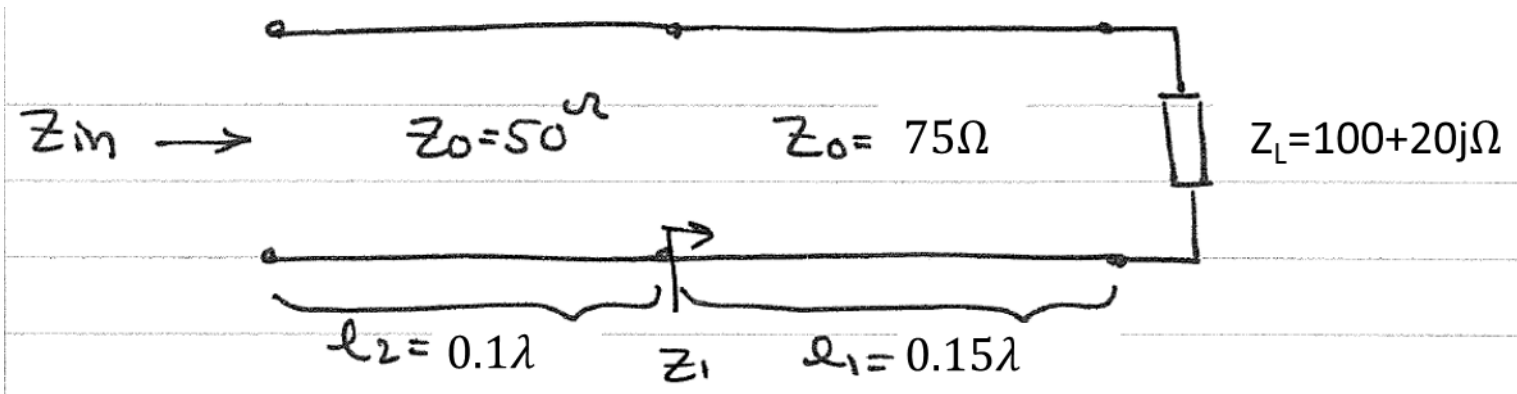- For the following circuit, (a) find the ABCD matrix via the Table 4.1 taught in class (b) find the S-parameter in ADS and convert it into ABCD matrix via Table 4.2. The operation frequency is at 1 GHz, $Z_0 = 50 \Omega$. $l = 0.1\lambda$. $Y = 100j$.



- Find the Z_1 and Z_{in} via (a) schematic in ADS and (b) Smith chart in ADS.



- Find the Z_1 and Z_{in} via (a) schematic in ADS and (b) Smith chart in ADS. $Z_L = 100 - 25j\Omega$. $C = 10$ pF. $L = 5$ nH. The operation frequency is at 1 GHz.

