

電磁波與天線導論 HW11

Name : 郭忠翔

ID : R10522845


1

$$50 - (30 + j40) = 20 - j40$$



impedance matching series R and C.

$$R = 20, \frac{1}{j\omega C} = -j40 \Rightarrow C = 1.657864(\text{pF}) - < \text{ans} >$$

Simulate in Smith Chart :

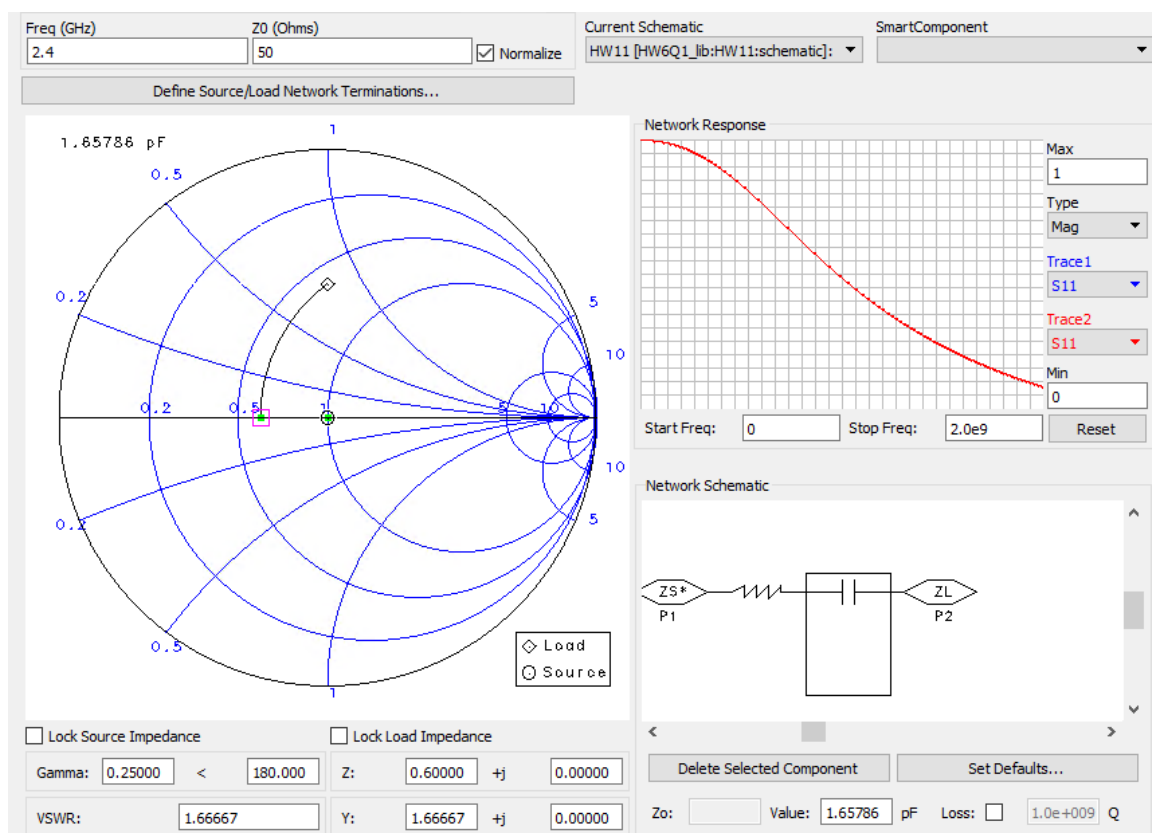


Model in ADS :

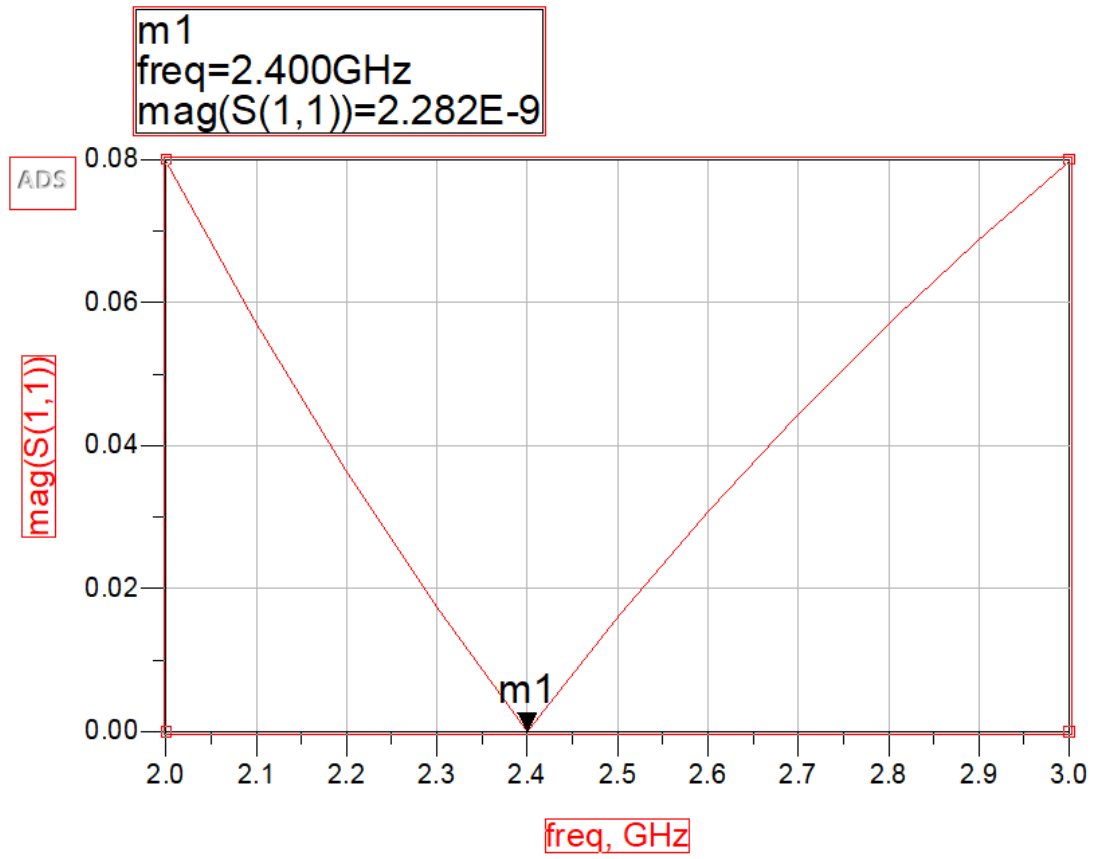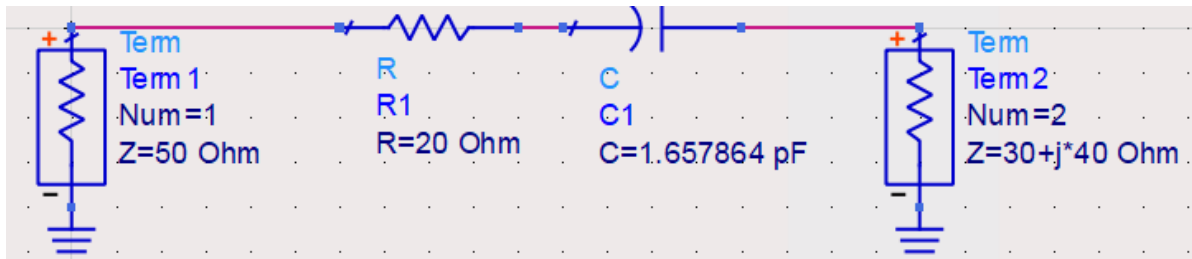


2

(a)

Rebuild in transmission line.

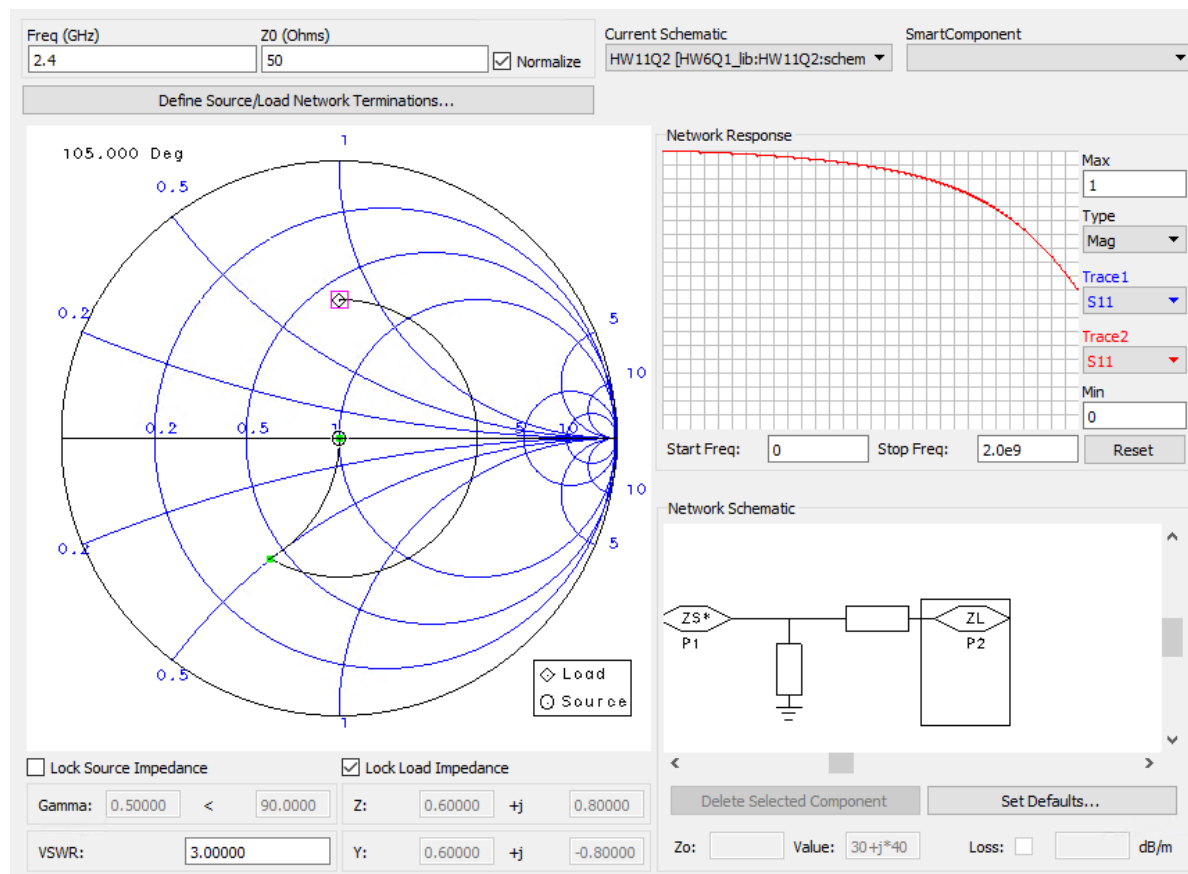

Covert to microstrip by line calculator.

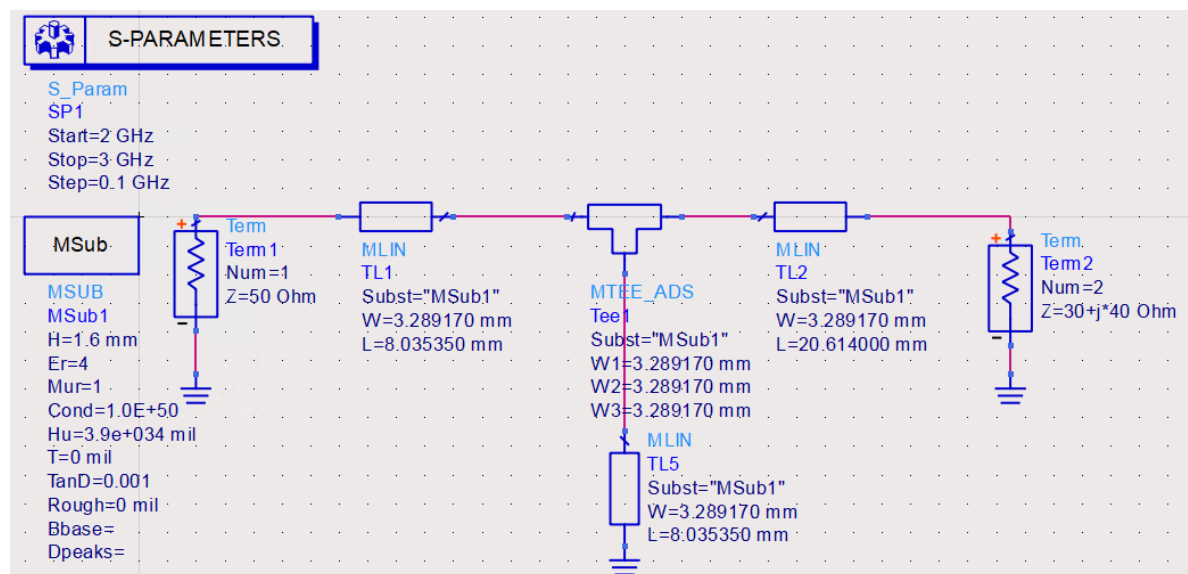

m1
freq=2.400GHz
dB(S(3,3))=-83.207

